

## Digital System Design

- At this point, we are trying to do complex datapaths + complex control
- Faced with problems of :
  - Constraints - minimum clock frequency, maximum number of clock cycles, target device, resource limits (don't have an infinite number of logic cells available)
  - Execution unit architecture and number : fast adder? Slow adder? Pipelined or non-pipelined multiplier? SRAM versus registers? How many do I need based on constraints?
  - Scheduling : what happens during what clock cycle?

BR 1/99

1

## Constraints

- Two **Constraints** that can be placed on a digital system design are clock period and clock cycle constraints
- A Clock period constraint will define the minimum clock frequency.
  - Will affect the architecture of your execution units (fast adder versus slow adder, pipelined execution unit versus non-pipelined execution unit)
- A clock cycle constraint limits the available number of clock cycles to perform operation
- Total computation time: clock period \* clock cycles
- Other constraints: Power, device type, Input/Output


BR 1/99

2
 
## Resource Estimation

- Given constraints, would like a lower bound estimate on the number of resources needed
- Resource types: Registers, Execution units (adders, multipliers, etc)
- Lets do resource estimation for the equation below:

$$Y = a_0 * x + a_1 * x@1 + a_2 * x@2 + a_3 * x@3$$



BR 1/99

3

## FIR Filter

$$Y = a_0 * x + a_1 * x@1 + a_2 * x@2 + a_3 * x@3$$

The equation above is an equation for a 4-Tap Finite Impulse Response digital filter.

Each *sample period* a new value for X is input to the system. A sample period is measured in clock cycles, and the number of clock cycles per sample period will be an external constraint.

X is the value for current sample period.  
 X@1 is the value for one sample period back.  
 X@2 is the value for two sample periods back.  
 X@3 is the value for three sample periods back.


A0, a1, a2, a3 are the filter coefficients. Changing these coefficients change the filter function; assumed to be preloaded.

BR 1/99

4
 
## Dataflow Graph

We need a method of visualizing the data dependencies and operations to be performed. One method of doing this is the *dataflow graph*.



BR 1/99

5

## Operations in a Dataflow graph



An input operation. Inputs are assumed registered. An input operation will take 1 clock cycle.



An output operation. Outputs are not assumed to be registered because they will be registered by the datapath they are being passed to! As such, they don't cost a clock cycle (its cycle cost is in the next datapath).




An execution unit operation. Based on clock period constraints, execution units can be **chained** (a multiplier output directly feeding an adder input without an intervening register) or **non-chained** (all inputs/outputs of execution units are registered).

BR 1/99

6
 
## What is minimum number of clock cycles needed?

Assume that clock period constraint does not allow execution unit chaining (registers are between execution units). Minimum # of clock cycles will be longest path through the datapath.



BR 1/99

7

## Resource Estimation

Given a clock cycle constraint (sample period), can estimate minimum number of needed resources.

Assume the minimum sample period of 4 clocks.

Minimum resource estimation is:

# operations/ # of clocks

Minimum Resource estimation:

# multipliers = # multiplies/ # clocks =  $4/4 = 1$

# adders = # additions/ #clocks =  $3/4 = 1$

Minimum resource estimation is 1 multiplier, 1 adder.

Register estimation is tougher. Need to store X@1, X@2, X@3 + four coefficients. Need at least 7 registers.

BR 1/99

8

## Scheduling

**Scheduling** is mapping operations onto execution units.

Use a scheduling table which lists clock cycles versus resources. Lets first just worry about execution units, and not about registers for now.

Resource: Cycle Start	Adder	Multiplier	IO
#1	idle	Reg?? ← x@3*a3 (N5)	Input X
#2	idle	Reg?? ← x@2*a2 (N4)	
#3	N7 op (N5+N4)	Reg?? ← x@1*a1 (N3)	
#4	idle	Reg?? ← x*a0 (N2)	

BR 1/99

9

## Scheduling Failed!

The scheduling failed! We were not able to schedule the adder operations represented by nodes N6 and N8.

The minimum resource estimation is a **lower bound**; may not find a schedule to fit it.

If scheduling fails, the two options:

- Increase resources, keep same # of clocks
- Increase # of clocks, keep same number of resources

We want a minimum sample period, so do option #a.

The bottleneck is the multiplier. Lets add another multiplier.

BR 1/99

10

## Scheduling (2nd try)

Resource: Cycle Start	Adder	Mult A	Mult B	IO
#1	idle	x@3*a3 (N5)	x@2*a2 (N4)	Input X
#2	N7 op (N5+N4)	x@1*a1 (N3)	x*a0 (N2)	
#3	N6 op (N3+N2)	idle	idle	
#4	N8 op (N7+N6)	idle	idle	

Scheduling succeeds.

BR 1/99

11

## Register Allocation

At this point, need to allocate registers to save temporary results. At beginning of operation, we know that we need to have the values a0,a1,a2,a3, x@3,x@2,x@1 stored. So we need at least 7 registers.

The registers holding a0-a3 will not change value during the computation, so we will not consider them in our scheduling.

Assume at Start: RA = x@3, RB=x@2, RC=x@1.

BR 1/99

12

## Register Scheduling (Clock #1)

Regs: RA = x@3, RB=x@2, RC=x@1.

Clock 1:

**Input X???** Where to put this? For now, use new register **RegD**.

Input X: RD ← X

x@3\*a3 (N5): RA ← RA \* a3 (don't need x@3 after this, destroy RA)

x@2\*a2 (N4): ??? ← RB \* a2 (will need x@2 next time, can't destroy RB!)

Add another register.

x@2\*a2 (N4) RE ← RB \* a2 (will need x@2 next time, can't destroy RB!)

Scheduling this operations forced us to add two additional registers (RD, RE).

Now do Clock #2

BR 1/99

13

## Register Scheduling (Clock #2)

Regs: RA = N5, RB=x@2, RC=x@1, RD=x, RE=N4

Clock 2:

N4 + N5 (N7): RA ← RE + RA (destroy RA, don't need N5 anymore)

x@1\*a1 (N3): ?? ← RC \* a1 (will need x@1 next time, can't destroy RC!)

Look for a free register. Don't need RE (N4) after this clock cycle, use it.

x@1\*a1 (N3): RE ← RC \* a1 (store result in RE).

x\*a0 (N2): ??? ← RD \* a0 (will need "x" next time, can't destroy RD!)

Any free registers? NO. Add another register.

x\*a0 (N2): RF ← RD \* a0

Scheduling these operations forced us to add one more register (RF).

Now do Clock #3

BR 1/99

14

## Register Scheduling (Clock #3, Clock #4)

Regs: RA = N7, RB=x@2, RC=x@1, RD=x, RE=N3, RF=N2

Clock 3:

N6 op (N3+N2) RE ← RE + RF (destroy RE, don't need N3 anymore)

Regs: RA = N7, RB=x@2, RC=x@1, RD=x, RE=N6, RF=N2

Clock 4:

N8 op (N7+N6) Yout ← RA + RE (output is unregistered)

What about initial conditions for next sample period? RA = x@3, RB=x@2, RC=x@1 ??

x@1 ← x

RC ← RD

Note that X in this sample period becomes X@1 for the next sample period, x@1 becomes x@2, etc...

x@2 ← x@1

RB ← RC

x@3 ← x@2

RA ← RB

BR 1/99

15

## Final Requirements

- For sample period = 4 clocks:
  - 2 Multipliers, 1 adder
  - 10 registers (RA-RF, plus 4 registers for a0,a1,a2,a3)
- Is this the best hardware allocation?
  - Maybe not, if we try harder may be able to remove a register or two.
- Lets go with this and try to build the datapath

BR 1/99

16

## Datapath Execution Unit sources, destinations

Mult A: Left sources: RA, RC

Right sources: a3, a1

Mult B: Left sources: RB, RD

Right sources: a2, a0

Adder: Left sources: RE, RA

Right sources: RA, RF, RE

RE

RA src: MultA, Adder, RB

RB src: RC

RC src: RD

RD src: X

RE src: Adder, Mult A, Mult B


RF src: Multiplier B

a0-a3 registers loaded from external databus X.

BR 1/99

17

## Datapath

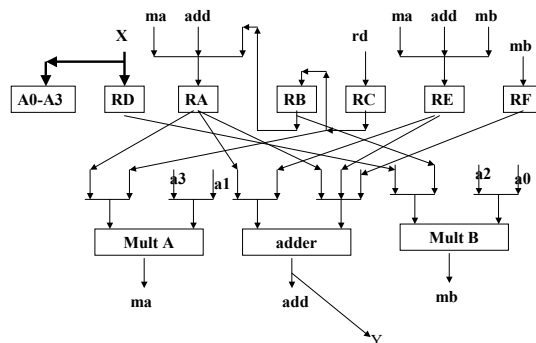

BR 1/99

18

### Comments

- Saving on Execution units leads to lots of wiring and muxes because of the amount of execution unit sharing that is required
- Could probably have reduced some of the mux requirements by more careful assignment of temporary values to registers
- This datapath would require a FSM with four states; each state corresponding to a clock cycle.
  - Output of FSM would be mux select lines, register load lines
  - May need extra states if handshaking control (input\_rdy, output\_rdy) is required.

BR 1/99

19

### Increasing number of available clocks

Lets increase sample period from 4 to 5, and see if we can get rid of multiplier.


Resource:	Adder	Multiplier	IO
Cycle Start			
#1	idle	Reg?? ← x@3*a3 (N5)	Input X
#2	idle	Reg?? ← x@2*a2 (N4)	
#3	N7 op (N5+N4)	Reg?? ← x@1*a1 (N3)	
#4	idle	Reg?? ← x@a0 (N2)	
#5	N6 op (N2 + N3)	idle	

BR 1/99

20
 
### Scheduling Still Failed

Did not schedule Node 8 (N8). There should be a way in which we can make better use of the adder. Try restructuring the flowgraph.



BR 1/99

21

### Try again with Sample Period = 5

Resource:	Adder	Multiplier	IO
Cycle Start			
#1	idle	Reg?? ← x@3*a3 (N5)	Input X
#2	idle	Reg?? ← x@2*a2 (N4)	
#3	N7 op (N5+N4)	Reg?? ← x@1*a1 (N3)	
#4	N6 op (N3+N7)	Reg?? ← x@a0 (N2)	
#5	N8 op (N2 + N6)	idle	

Scheduling succeeds with new flowgraph!!!!!!

BR 1/99

22

### Flowgraph for Matrix Multiply

$$\begin{pmatrix} T00 & T01 & T02 & T03 \\ T10 & T11 & T12 & T13 \\ T20 & T21 & T22 & T23 \\ T30 & T31 & T32 & T33 \end{pmatrix} \begin{pmatrix} X \\ Y \\ Z \\ W \end{pmatrix}$$


$$\begin{aligned} X' &= X*T00 + Y*T01 + Z*T02 + W*T03 \\ Y' &= X*T10 + Y*T11 + Z*T12 + W*T13 \\ Z' &= X*T20 + Y*T21 + Z*T22 + W*T23 \\ W' &= X*T30 + Y*T31 + Z*T32 + W*T33 \end{aligned}$$

IO Constraint: Single input bus, single output bus

BR 1/99

23

### Flowgraph for Matrix Multiply (cont)

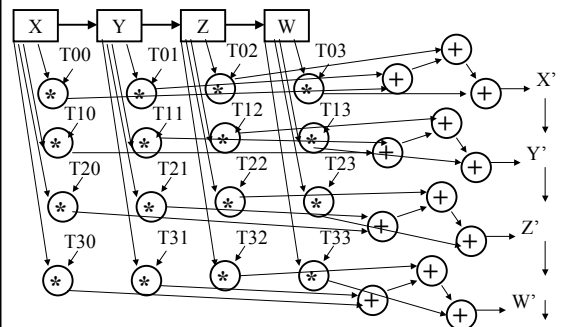

BR 1/99

24


## Comments on MM Flowgraph

- The main thing to notice about the graph is that you don't have to wait until you have X,Y,Z,W before you begin operations
  - Once you have X, you can do four multiply operations
- Another thing to note is the symmetry and parallelism available
  - You could have four parallel datapaths, each one containing a multiplier and an adder, and produce X', Y', Z', W' from these four datapaths

BR 1/99

25

## Parallel Datapaths for MM

 

BR 1/99

26

## On Latency, Initiation Rate

**Initiation Rate:** Rate at which new values are input


**Latency:** Number of clocks from input value to COMPLETED output value

For the project, initiation rate will be number of clocks from inputting X for one set of (X,Y,W,Z) to inputting the next X for a new set of (X,Y,W,Z)

BR 1/99


27

## Defining Initiation Rate, Latency

 


BR 1/99

28

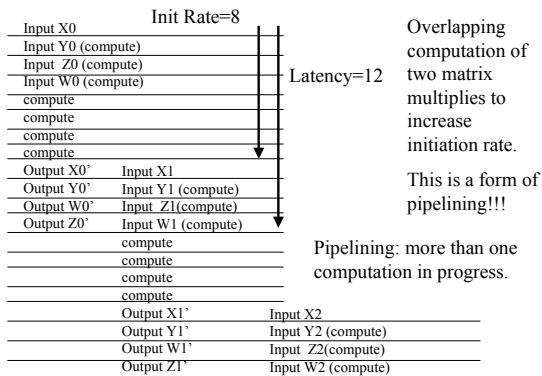

BR 1/99

29

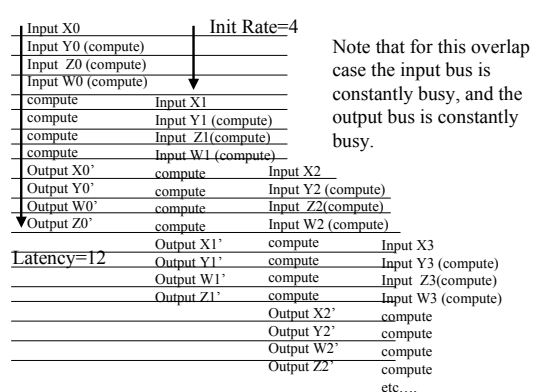

BR 1/99

30