 


Modeling Complex Behaviors: Synthesis

VHDL Synthesis

VHDL Model


```
entity my_ckt is
port(x, y:in bit;
      z: out bit)
end entity my_ckt;
architecture behavioral of my_ckt is
begin
--
-- process code here
--
end architecture behavioral;
```



- Inferring hardware from sequential code in processes
 - Multiple alternative implementations
 - Metrics for selecting the right implementation
- Coding style can “help” the compiler

Language Directed View

 - Inferring combinational logic
 - Every combination of inputs produces an output
 - Every execution path performs an assignment to every signal



- Inferring sequential logic
 - A signal is not assigned in some execution path
- ➡ remember the value, i.e., storage

ECE 4170 (3)

Simple Assignment Statements

```

architecture behavior of stover is
  signal sig_s1, sig_s2: std_logic;
begin
  proc1: process (x, y, z) is -- Process 1 using variables
    variable var_s1, var_s2: std_logic;
  begin
    var_s1 := x and y;
    var_s2 := var_s1 xor z;
    res1 <= var_s1 and var_s2;
  end process proc1;

```

```

proc2: process (x, y, z) -- Process 2 using signals

```

```

begin
  sig_s1 <= x and y;
  sig_s2 <= sig_s1 xor z;
  res2 <= sig_s1 and sig_s2;
end process proc2;


```

```

end architecture behavior;

```

 - Simulation mismatch
 - synthesis collapses multiple simulation cycles
- Dependence analysis



ECE 4170 (4)

Conditional Statements

architecture behavior of inflate is

begin

process (x, y, z, sel) is

variable s1, s2: std_logic;

begin

if (sel = '1') then

s1 := x and z;


s2 := s1 xor y;

w <= s2 and s1; -- w gets a value only conditionally

end if; -- hence a latch is inferred

end process;

end architecture behavior;

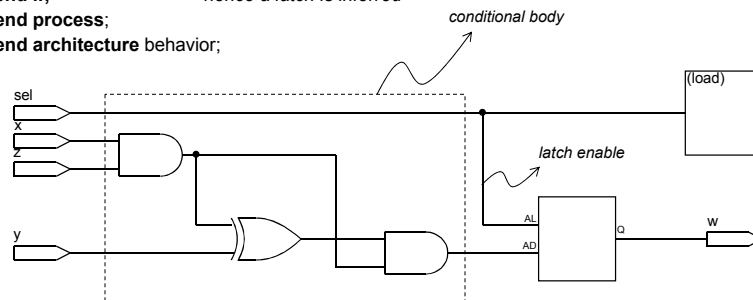

ECE 4170 (5)

Avoiding Latch Inference

- Ensure every path computes a value for every signal
 - Presence of the else branch
 - Nested structures
 - if-then-elsif structure
- Use initial values
- Basic principle: ensure that every combination of input signal values leads to a computation of a value for every output signal



combinational logic


ECE 4170 (6)

Revisit the Example

```

architecture behavior of inflate is
begin
  process (x, y, z, sel) is
    variable s1, s2: std_logic;
  begin
    w <= '0'; -- output signal set to a default value to avoid latch inference
    if (sel = '1') then
      s1 := x and z; -- body generates combinational logic
      s2 := s1 xor y;
      w <= s2 and s1;
    end if;
  end process;
end architecture behavior;


```

 

ECE 4170 (7)

Efficiency Considerations

 - Now that we can control latch inferencing what about circuit size and speed?
- Move common operations (hardware) out of the branches
 - Good programming practice in general
 - Trade multiplexors for more expensive hardware




ECE 4170 (8)

Efficiency Considerations

```
library IEEE;
use IEEE.std_logic_1164.all;
entity inference is
port (sel : in std_logic;
      x, y, z : in std_logic;
      w : out std_logic);
end entity inference;
```
 
```
architecture behavior of inference is
begin
process (x, y, z, sel) is
begin
if (sel = '1') then
w <= x and y;
else
w <= x and z;
end if;
end process;
end architecture behavior;
```




- Eliminated the latches
- Computation (logical AND) preceded by operand selection (mux)



```
library IEEE;
use IEEE.std_logic_1164.all;
entity inference is
port (sel : in std_logic;
      x, y, z : in std_logic;
      w : out std_logic);
end inference;
```
 
```
architecture behavior of inference is
begin
process (x, y, z, sel)
variable right: std_logic;
begin
if (sel = '1') then
right := y;
else
right := z;
end if;
w <= x and right;
end process;
end behavior;
```




ECE 4170 (9)

Nested Constructs

architecture behavior of nested_if is
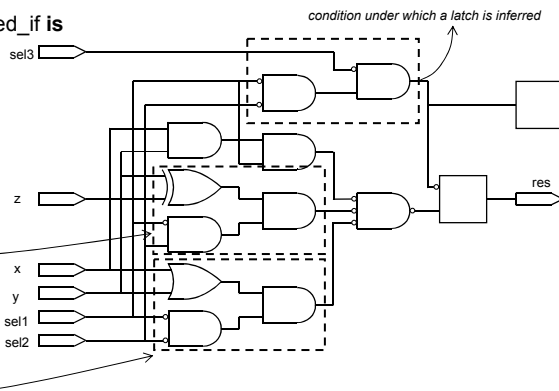
```
begin
process (x,y,z,sel1,sel2,sel3)
begin
if (sel1 = '1') then
res <= x and y;
elsif (sel2 = '1') then
res <= y xor z;
elsif (sel3 = '1') then
res <= x or y;
end if;
end process;
```



- Latch inference due to the absence of the last "else"
- Latch inference due to placement in higher level blocks
- Priority ordering of the computations

ECE 4170 (10)

Comparison Logic and Effects

```

architecture behavior of stover is
begin
  process (x, y, z) is
  begin
    if (sel = "-- 0") then      -- the symbol "--" represents the don't care
    w <= x nor y;              -- for std_logic types
    else
    w <= x nor z;
    end if;

  end process;
end architecture behavior;

```

- Comparison always returns false - the "then" branch is never taken
- Synthesis returns the combinational logic for the "else" branch – a single NOR gate


ECE 4170 (11)

CASE Statements

```

architecture behavior of case_st is
begin
  process (x,y,z,sel) is
  begin
    case sel is
    when 0 => res <= x and y;
    when 1 => res <= y xor z;
    when 2 => res <= x nand z;
    when others => res <= x nor z;
    end case;
  end process;
end architecture behavior;

```

 


- Synthesis of a multiplexor
- Latch inference intuition applies
- Difference with nested *if-then-elsif* → latter synthesizes priority logic

ECE 4170 (12)

CASE Statements (cont.)

architecture behavior of case_ex is
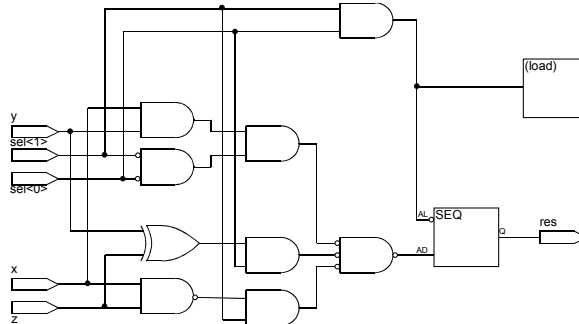
```
begin
process (x,y,z,sel) is
begin
case sel is
when 0 => res <= x and y;
when 1 => res <= y xor z;
when 2 => res <= x nand z;
when others => null;
-- in this case the value of res
-- remains unaltered
end case;
end process;
end architecture behavior;
```



- Use of the “null” statement and latch inference

ECE 4170 (13)

Loop Statements

- How much hardware should be generated?
- Most commonly supported is the *for loop*
 - Number of iterations is known a priori
 - Loop is unrolled and optimized as a sequence of sequential statements

```
for N in 3 downto 1 loop
shift_reg (n) <= shift_reg (n-1);
end loop;
```



```
shift_reg (3) <= shift_reg (2);
shift_reg (2) <= shift_reg (1);
shift_reg (1) <= shift_reg (0);
```

- Dependencies within and across iterations
 - Cross iteration dependencies synthesize to long signal paths
- Constraints on type of loop index

ECE 4170 (14)

Loop Statements: Example


```

architecture behavior of iteration is
  signal shift_reg : std_logic_vector(3 downto 0);
  begin
    process (clk, reset, data) is
      begin
        if (rising_edge(clk)) then
          if (reset = '1') then res <= "0000";
          else
            for n in 3 downto 1 loop
              shift_reg(n) <= shift_reg(n-1);
            end loop;
            shift_reg(0) <= data;
            res <= shift_reg;
          end if;
        end if;
      end process;
    end architecture behavior;
  
```

- Call to rising_edge(clk) produces edge triggered flip flops
- Loop leads to sequence of dependent assignment statements

ECE 4170 (15)


Loop Statements: Example

 

ECE 4170 (16)

Miscellaneous Issues

 - Use of sensitivity lists: all signals are in the sensitivity list for synthesis



- Pre-synthesis and post-synthesis simulation mismatches
- Optimizations involving variables
 - Eliminate intermediate variables
- Architecture level interpretation of inference rules
 - Latch inference occurs at outermost level of inferencing
- Use of *buffer* and *inout* modes.

ECE 4170 (17)

Inference Using Signals vs. Variables

```
library IEEE;
use IEEE.std_logic_1164.all;
```

```
entity sig_var is
port (sel : in std_logic;
      x, y, z: in std_logic;
      v, w: out std_logic);
end entity sig_var;
```

```
architecture behavior of sig_var is
signal sig_s1 : std_logic;
begin
process (x, y, z, sel) is
variable var_s1: std_logic;
```


```
L1: if (sel = '1') then
sig_s1  <= x and z;
v       <= sig_s1 xor y;
end if;
```

```
L2: if (sel = '0') then
var_s1  := x and z;
v       <= var_s1 xor y;
end if;
end process;
end architecture behavior;
```

- Variable synthesized to a wire vs. signal synthesized to a latch
- Why is a latch inferred at all since all execution paths are covered?

ECE 4170 (18)

Inference Using Signals vs. Variables

 

- Current value (variable) vs. previous value (signal)

ECE 4170 (19)


Inferring Storage for Variables

```

architecture behavior of sig_var is
begin
  process
    variable var_s1, var_s2 :std_logic;
  begin
    wait until (rising_edge(clk));
    var_s1 := x nand var_s2;
    var_s2 := var_s1 xor y;
    res <= var_s1 xor var_s2;
  end process;
end behavior;

```

 - Variables used before it is defined
 - Variables retain values across invocations
- There exists an execution sequence (first) where use precedes definition



ECE 4170 (20)

Latch vs. Flip Flop Inference

- Predicates in conditional expressions lead to latch inference
 - *if (sel = '1') then...*
 - Edge detection expressions lead to flip flop inference
 - *if (rising_edge(clk)) then...*
 - *if (clk'event and clk = '0') then..*
 - *if (clk'lastvalue = '0' and clk = '1' and clk'event) ..*
- simulation semantics only*
- Semantics must be consistent with available parts
 - Latches vs. flip flops
 - Trigger condition

Example: Counter

```


entity counter is
  port (clk, reset : in std_logic;
        res : out unsigned (3 downto 0));
end entity counter;

architecture behavior of counter is
  begin
    process (clk, reset) is
      variable var_count : unsigned (3 downto 0);
      begin
        if (rising_edge (clk)) then
          if (reset = '1') then res <= "0000";
        else
          var_count := var_count + 1;
        end if;
        res <= var_count;
      end if;
    end process;
  end architecture behavior;
  
```

edge trigger

Note variable is used before it is defined!

Example: Counter

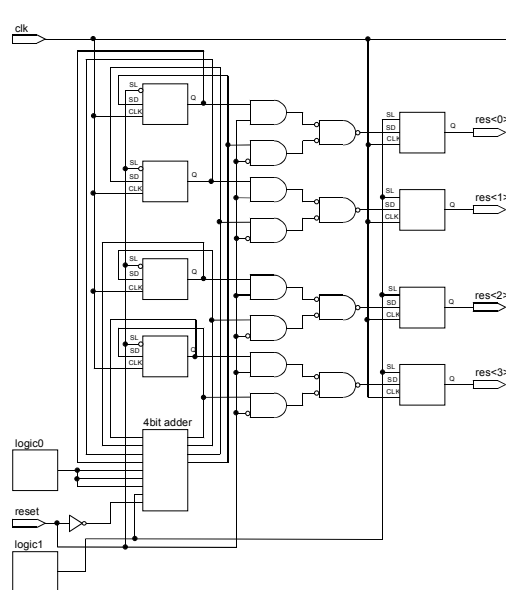

ECE 4170 (23)

Wait Statements

- Wait statements imply synchronous logic
- Only one wait statement permitted in a process and it must be the first statement in the process
- All signals in the body of the wait cause storage to be inferred
- Use *if-then-elsif-endif* constructs to trade-off combinational vs. sequential circuit inference

ECE 4170 (24)

Controlling Inference: Example

```

architecture behavioral of edge is
begin
  process
  begin
    wait until (rising_edge(clk));
    if reset = '1' then
      Aout <= 1;
    else
      Aout <= 3;
    end if;
    Bout <= 0;
  end process;
end architecture behavioral;

```


```

architecture behavioral of edge is
begin
  process (reset, clk) is
  begin
    if reset = '1' then
      Aout <= 1;
    else
      Aout <= 3;
    end if;
    if (rising_edge(clk)) then
      Bout <= 0;
    end if;
  end process;
end architecture behavioral;

```

- Control inference by use of the wait statement

Controlling Inference: Example

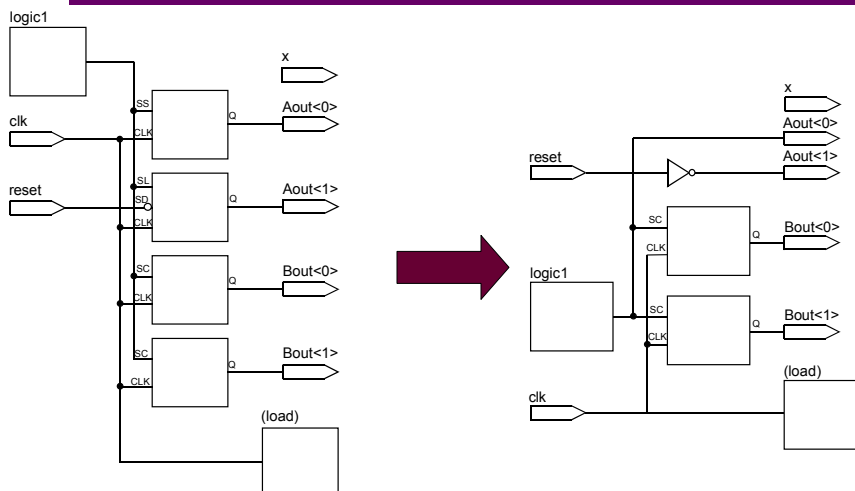

- Storage inference is a function of code structure

Simulation vs. Synthesis Semantics

Consistency with simulation semantics?

```
wait until rising_edge (clk);
sig_a <= sig_x and sig_y;
sig_b <= sig_a xor sig_c;
```

- What value of sig_a is used in the computation of sig_b?

Consistency with simulation semantics?

```
process (x, y, z)
begin
L1: s1 <= x xor y;
L2: s2 <= s1 or z;
L3: w <= s1 nor s2;
end process;
```


- Storage is not inferred in this example!

ECE 4170 (27)

Variables Controlled by a Wait Statement

```
library IEEE;
use IEEE.std_logic_1164.all;
entity sigvar is
port(y, z, x, clk : in std_logic;
     res: out std_logic);
end entity sigvar;

 
architecture behavioral of sigvar is
begin
process is
variable a_var, b_var : std_logic;
begin
wait until (rising_edge(clk));
a_var := x or y;
b_var := a_var nor z;
res <= b_var xor y;
end process;
end architecture behavioral;
```



- Variable dependencies collapsed
- If variables are “used before they are defined” then storage is inferred
- Signal dependencies are not collapsed, but rather storage is inferred for each signal

ECE 4170 (28)

Synthesis of State Machines

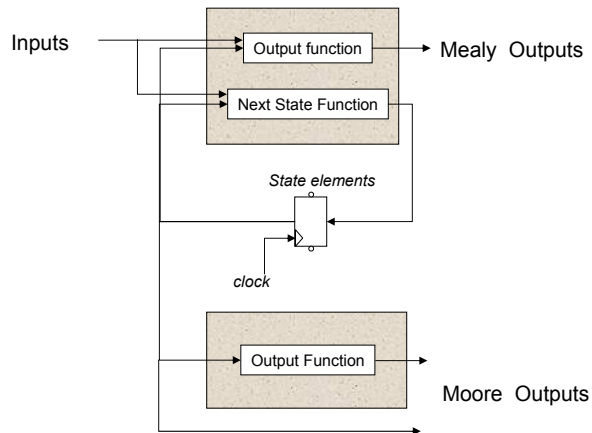

- Combinatorial component and sequential component
- Asynchronous and synchronous components
- Control inference through use of wait and edge detection expressions

ECE 4170 (29)

State Encodings

State	Sequential	Gray Code	One Hot
0	000	000	00000001
1	001	001	00000010
2	010	011	00000100
3	011	010	00001000
4	100	110	00010000
5	101	111	00100000
6	110	101	01000000
7	111	100	10000000

- Source-level constructs for user supplied encodings
- Goal: optimize area or speed
- What about illegal states?

ECE 4170 (30)

Controlling Inference: Example

architecture behavioral of state_machine is

type statetype is (state0, state1);

signal state, next_state : statetype ;

begin

process is

begin

wait until (rising_edge(clk)); -- rising edge

if reset = '1' **then**

res <= '0'; -- check for reset

state <= statetype'left; -- initialize state

else

case state is -- switch on current state

when state0 => -- set outputs and next state

if x = '0' **then**

state <= state1;

res <= '1';

else state <= state0;

res <= '0';

end if

when state1 =>

if x = '1' **then**

state <= state0;

res <= '0';

else

state <= state1;

res <= '1';

end if;

end case;

end if;


end process;

end architecture behavioral;

- Flips flops inferred for all signals in the body of the process

ECE 4170 (31)

Controlling Inference: Example

 

ECE 4170 (32)



Controlling Inference: Example

```
architecture behavioral of state_machine is
type statetype is (state0, state1);
signal state, next_state : statetype;
begin
process (state, x) is
begin
case state is -- switch on the current state
when state0 => -- set output and next state
if x = '0' then
next_state <= state1;
res <= '1';
else
next_state <= state0;
res <= '0';
end if;
when state1 =>
if x = '1' then
next_state <= state0;
res <= '0';
```

```
else
next_state <= state1;
res <= '1';
end if;
end case;
end process;
```


```
clk_process: process is
begin
wait until (rising_edge(clk));
if reset = '1' then -- reset and initialize
state <= statetype'left;
else
state <= next_state;
end if;
end process clk_process;
end architecture behavioral;
```

- Flip flops for the signal “res” are avoided

ECE 4170 (33)



Simulation vs. Synthesis

 

- Design flow transforms a design to more detailed levels
- Simulation at each level to validate design
- Need to understand sources of mismatch between levels
- Performance issues differ at each level

ECE 4170 (34)

- Obvious source: design error
- Incomplete sensitivity lists

```
process (sel) is
begin
  if (sel = '1' and En = '0') then
    A <= 1;
  else
    A <= '0';
  end if;
end process;
```

- Use of signals in a process

```
process (x, y, z)
begin
  L1: s1 <= x xor y;
  L2: s2 <= s1 or z;
  L3: w <= s1 nor s2;
end process;
```

- Delay statements
- Speed
 - Overhead of maintaining and updating signal drivers
 - Use of processes and variables speed up simulation


Some Synthesis Guidelines: From Xilinx

- Use of resets
 - Asynchronous resets can prevent inference of optimized components
 - Optimized SRL library does not have reset
 - Building SRLs places reset on the critical path
 - Only synchronous resets available on some components
 - Mapping general logic to RAM
 - Efficiency of inference
 - Use synchronous reset as possible and necessary
 - Use of asynchronous resets results in synthesis of additional logic outside of primitives
 - Interferes with remainder of the design, e.g. during place and route
 - Optimizations for synchronous reset and logic synthesis

From <http://www.xilinx.com/bvdocs/whitepapers/wp231.pdf>

ECE 4170 (37)

Some Synthesis Guidelines: From Xilinx

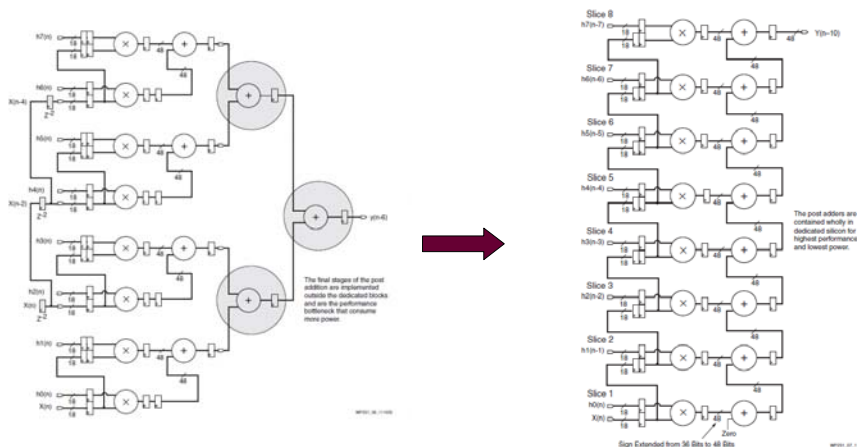

- Trading throughput for latency
 - Adder chains vs. adder trees

From <http://www.xilinx.com/bvdocs/whitepapers/wp231.pdf>

ECE 4170 (38)



Some Synthesis Guidelines: From Xilinx


- Using registers
 - Pipelining for throughput
 - Can be coupled with retiming to further improve performance
 - What happens to our ability to verify circuits?
 - Register replication to handle high fan out
- Instantiation vs. inference
 - Some optimized behaviors cannot be inferred (in today's compilers)
 - Boundaries of optimization
 - “cone of influence” from instantiated components
 - Sometimes easier to instantiate elements than describe them effectively
 - e.g., Serdes

From <http://www.xilinx.com/bvdocs/whitepapers/wp231.pdf>

ECE 4170 (39)



Some Synthesis Guidelines: From Xilinx

 

- Clock gating vs. enables with global resources

From <http://www.xilinx.com/bvdocs/whitepapers/wp231.pdf>

ECE 4170 (40)



Some Synthesis Guidelines: From Xilinx

- Nesting
 - Avoid deep nesting which leads to long signal paths
 - Can explicitly place registers in a loop to avoid long signals in unrolled loop
- Hierarchy
 - Boundaries may have to be preserved for verification purposes
 - Use global resources at the highest level of the hierarchy
- Check for additional resources in the document and Xilinx website for more info

From <http://www.xilinx.com/bvdocs/whitepapers/wp231.pdf>

ECE 4170 (41)



Coding Styles

- Target independent vs. target dependent coding style
- Keep synthesizable blocks relatively small
- Separate combinational from clocked (registered) pieces of logic
 - Use nested if-then-elsif-endif structure in process followed by edge detected blocks of code
- Check
http://toolbox.xilinx.com/docsan/xilinx7/books/data/docs/sim/sim0026_6.html

ECE 4170 (42)

- Synthesis of behaviors encapsulated in processes
- Inference from sequential statements
- Latch inference vs. flip flop inference
- Effect of using variable vs. signals for synthesis
- Inference using *wait* vs. *if-then-else* statements
- Optimizations